

## Homework 4

1. Textbook Problems 4.37: Write the HDL gate-level hierarchical description of a four-bit adder-subtractor for unsigned binary numbers. The circuit is similar to Fig.4.13 but without output V. You can instantiate the four-bit full adder described in HDL Example 4.2. (see Problems 4.13 and 4.40.) Write a test bench to test your module.

*4bit\_adder\_subtractor.v*

```
module half_adder(output S, C, input x, y);
    // Instantiate primitive gates
    xor (S, x, y);
    and (C, x, y);
endmodule

module full_adder(output S, C, input x, y, z);
    wire S1, C1, C2;

    // Instantiate half_adders
    half_adder HA1 (S1, C1, x, y);
    half_adder HA2 (S, C2, S1, z);
    or G1 (C, C2, C1);
endmodule

module ripple_carry_4_bit_adder(output [3:0] Sum, output C4,
    input [3:0] A, B, input C0);

    wire C1, C2, C3;    // Intermediate Carries

    // Instantiate full_adders
    full_adder FA0 (Sum[0], C1, A[0], B[0], C0),
                FA1 (Sum[1], C2, A[1], B[1], C1),
                FA2 (Sum[2], C3, A[2], B[2], C2),
                FA3 (Sum[3], C4, A[3], B[3], C3);
endmodule
```

*4bit\_adder\_subtractor\_tb.v:*

```
module four_bit_adder_subtractor_tb;
    // Inputs
    reg [3:0] A;
    reg [3:0] B;
```

```

reg Cin;

// Outputs
wire Cout;
wire [3:0] Sum;

// Instantiate the Unit Under Test (UUT)
ripple_carry_4_bit_adder uut(.Sum(Sum), .C4(Cout), .A(A), .B(B),
.C0(Cin));

initial
begin
    $display("Time\t A \t B \t Cin \t | Sum \t Cout");
    $monitor("%3g\t %b \t %b \t %b \t | %b  %b", $time, A, B,
Cin, Sum, Cout);

end

initial
begin

    A = 0000; B = 0001; Cin = 0;
    #10 A=0100; B=1011; Cin=0;
    #10 A=1000; B=0010; Cin=0;
    #10 A=0100; B=0011; Cin=1;
    #10 A=1100; B=0011; Cin=1;
    #10 A=1100; B=0100; Cin=1;
    #10 A=0100; B=0000; Cin=0;
    #10 A=0100; B=0001; Cin=0;
    #10 A=0100; B=0010; Cin=0;
    #10 A=0100; B=0000; Cin=1;
    #10 A=0100; B=0001; Cin=1;
    #10 A=0100; B=0010; Cin=1;

    #10 $finish;

end
endmodule

```

Output:

Time	A	B	Cin	Sum	Cout
0	0000	0001	0	0001	0
10	0100	0011	0	0111	0
20	1000	1010	0	0010	1
30	0100	1011	1	0000	1
40	1100	1011	1	1000	1
50	1100	0100	1	0001	1
60	0100	0000	0	0100	0
70	0100	0001	0	0101	0

80	0100	1010	0		1110	0
90	0100	0000	1		0101	0
100	0100	0001	1		0110	0
110	0100	1010	1		1111	0

## 2. Textbook Problems 4.13 (p.184):

**4.13\*** The adder–subtractor circuit of Fig. 4.13 has the following values for mode input  $M$  and data inputs  $A$  and  $B$ .

	$M$	$A$	$B$
(a)	0	0111	0110
(b)	0	1000	1001
(c)	1	1100	1000
(d)	1	0101	1010
(e)	1	0000	0001

In each case, determine the values of the four  $SUM$  outputs, the carry  $C$ , and overflow  $V$ . (HDL—see Problems 4.37 and 4.40.)

(a)

Cin = 0	C3	C2	C1	C0
	1	1	0	0
A	0	1	1	1
B	0	1	1	0
A + B = Cout = 0	1	1	0	1

Sum = 1101

$$C = \text{Cout} = 0$$

$$V = (\text{Cout} \wedge C3) = 0 \wedge 1 = 1$$

(b)

C <sub>in</sub> = 0	C3	C2	C1	C0
	0	0	0	0
A	1	0	0	0
B	1	0	0	1
A + B = Cout = 1	0	0	0	1

$$\text{Sum} = 0001$$

$$C = \text{Cout} = 1$$

$$V = (\text{Cout} \wedge C3) = (1 \wedge 0) = 1$$

(c)

C <sub>in</sub> = 1	C3	C2	C1	C0
	1	1	1	1
A	1	1	0	0
B	0	1	1	1
A + B = Cout = 1	0	1	0	0

$$\text{Sum} = 0111$$

$$C = \text{Cout} = 1$$

$$V = (\text{Cout} \wedge C3) = (1 \wedge 1) = 0$$

(d)

C <sub>in</sub> = 1	C <sub>3</sub>	C <sub>2</sub>	C <sub>1</sub>	C <sub>0</sub>
	1	0	1	1
A	0	1	0	1
B	0	1	0	1
A + B = C <sub>out</sub> = 0	1	0	1	1

Sum = 1011

C = C<sub>out</sub> = 0

V = (C<sub>out</sub> ^ C<sub>3</sub>) = (0 ^ 1) = 1

(e)

C <sub>in</sub> = 1	C <sub>3</sub>	C <sub>2</sub>	C <sub>1</sub>	C <sub>0</sub>
	0	0	0	0
A	0	0	0	0
B	0	0	0	1
A + B = C <sub>out</sub> = 0	1	1	1	1

Sum = 1111

C = C<sub>out</sub> = 0

V = (C<sub>out</sub> ^ C<sub>3</sub>) = (0 ^ 0) = 0

### 3. Textbook Problems 4.44:

**4.44** Using a case statement, write an HDL behavioral description of a eight-bit arithmetic-logic unit (ALU). The circuit has a three-bit select bus (Sel), sixteen-bit input datapaths (A[15:0] and B[15:0]), an eight-bit output datapath (y[15:0]), and performs the arithmetic and logic operations listed below.

Sel	Operation	Description
000	$y = 8'b0$	
001	$y = A \& B$	Bitwise AND
010	$y = A   B$	Bitwise OR
011	$y = A \wedge B$	Bitwise exclusive OR
100	$y = \sim A$	Bitwise complement
101	$y = A - B$	Subtract
110	$y = A + B$	Add (Assume A and B are unsigned)
111	$y = 8'hFF$	


*ALU.v:*

```
module ALU ( output [7:0] Y, input[7:0] A, B, input [2:0] Sel);  
    always @ (A, B, Sel)  
    begin  
        y = 0;  
        case (Sel)  
            3'b000: y = 8'b0;  
            3'b001: y = A & B;  
            3'b010: y = A | B;  
            3'b011: y = A ^ B;  
            3'b100: y = A + B;  
            3'b101: y = A - B;  
            3'b110: y = ~A;  
            3'b111: y = 8'hFF;  
        endcase  
    end  
endmodule
```

~

4. Design a binary sequence detector that detects the sequence *000*. Overlap is allowed. You may use either D flip-flops or JK flip-flops. Write a Verilog program to verify your design.

(i) State Diagram

 

(ii) Assign States

$Q_1, Q_0$

(iii) State Table

$Q_1(t)$	$Q_0(t)$	$I(t)$	$Q_1(t + 1)$	$Q_0(t + 1)$	$F(t)$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	0	0	1
0	1	1	0	1	0
1	0	1	1	0	0

Using D flip-flops:

$$D_0 = Q_1\bar{I} + Q_0I$$


$I \backslash Q_1Q_2$	00	01	11	10
0	0	0	X	1
1	0	1	X	0

$$D_1 = \overline{Q_1} * \overline{Q_0} * \bar{I} + Q_1I$$

$I \backslash Q_1Q_2$	00	01	11	10
0	1	0	X	0
1	0	0	X	1

(iv) Circuit Diagram:



 

**Self-Evaluation:** I have answered every question in this homework assignment to the best of my ability. I would give myself the maximum points allowed for this assignment which is 55 points.